

ELEN 50 Lab 4
Bradley Lostak
Tamir Enkhjargal
Friday 2:15-5:00p

Prelab:

Part 1: R_1 should be 1.25 k Ω .

Part 2: R_1 should be 1 k Ω .

Part A:


2) Output voltage = -12.4V

3) DC Voltage gain = $\frac{-12.4}{1} = -12.4$


4) Current = 0.00084 mA, $\frac{1}{0.00084} = 1190.5 \sim 1.2\text{k}\Omega$

5) Error Voltage = -2.6304 V

6) Using Amplitude of 1 Vpp

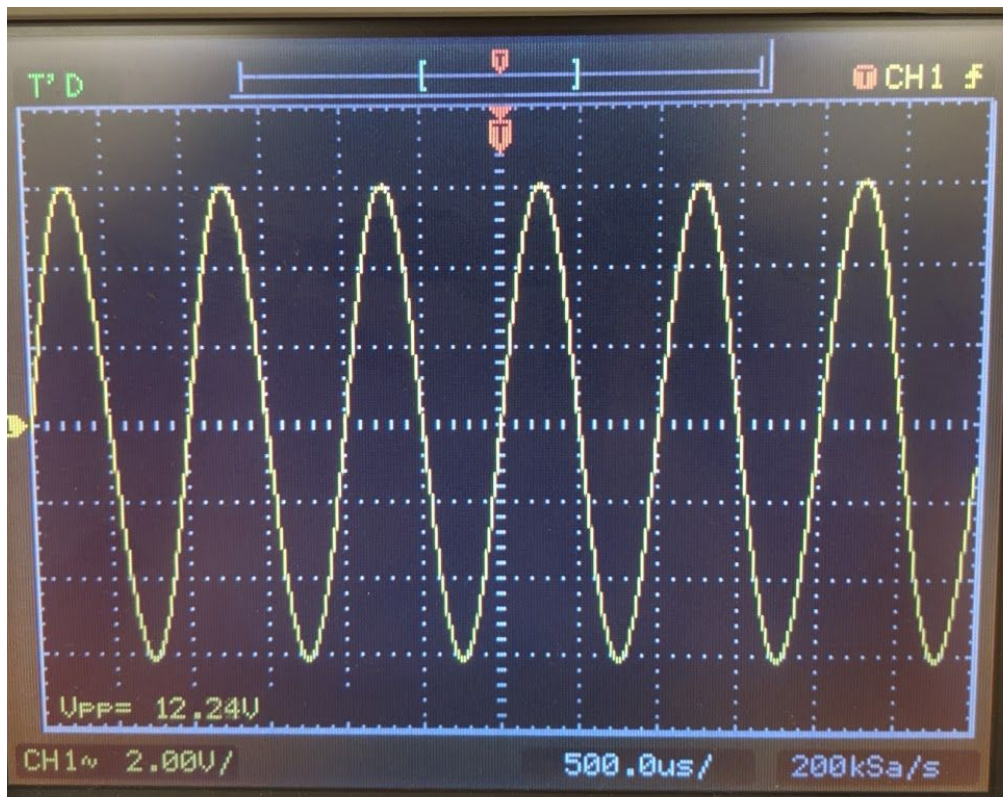

Using Amplitude of 3 Vpp

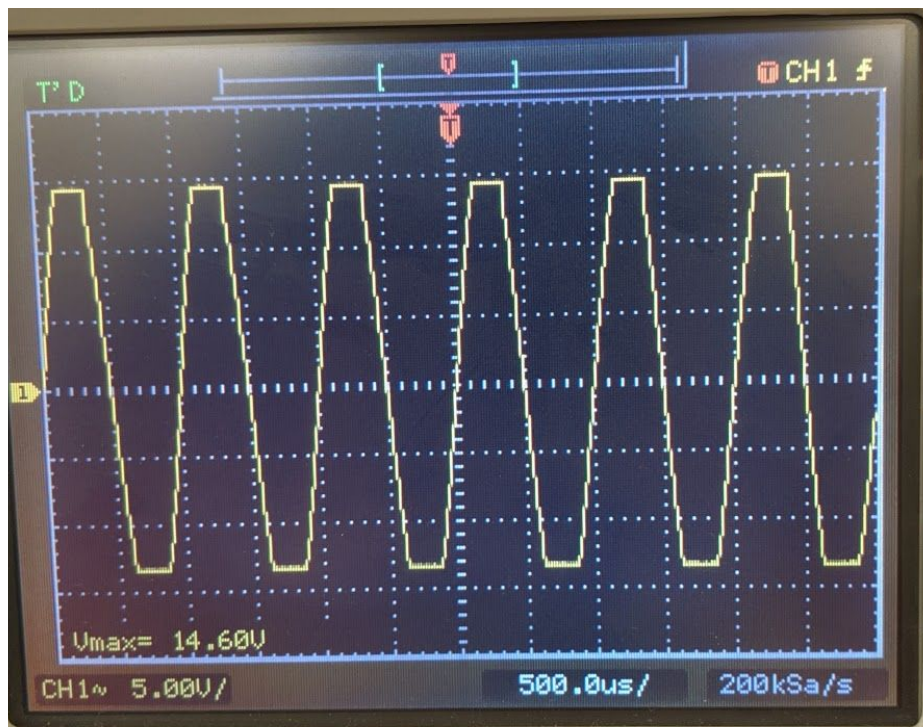

The graph looks like this because it can't go larger than the input $\pm V_{cc}$ (+15,-15). Once it goes above the V_{cc} magnitude, the circuit becomes negatively and positively saturated.

Part B:

510 Ω R :

- .514 V DMM
- .507 V Op Amp
- Percentage Error: .028%

1K Ω R:

- .987 V DMM
- .994 V Op Amp
- Percentage Error: .71%

3.9K Ω R:

- 3.915 V DMM
- 3.911 V Op Amp
- Percentage Error: .102 %

5.1k Ω R:

- 5.083 V DMM
- 5.064 V Op Amp
- Percentage Error: .374%

10k Ω R:

- 10.104 V DMM
- 10.067 V Op Amp
- Percentage Error: .366%