

ELEN 21 Lab 9: Shift Register Based One
Dimensional Pong Game
Pre-Lab

Tamir Enkhjargal
November 2018

II. Pre-Lab

For the prelab design a part of the controller for the pong game that has very limited operation. Only one player can serve and neither player can use a paddle. The controller should do the following:

- Reset to an *Idle* state and wait for a serve input when a reset signal is received.
- Respond to a serve input from the right side by going to the *Right Serve* state which places the ball at the appropriate serial input of the 16-bit shift register.
- From the *Right Serve* state the system goes to the *Move Left* state on the next active clock edge. In this state the ball moves across the 16 LEDs of the “game table”, advancing one LED on each clock edge.
- If the ball exits the shift register without being returned by a paddle, which will always happen here because this limited system does not have paddles, the system goes to the *End Left* state. This state holds the ball outside the shift register. The system stays in this state until another serve input comes from the right side which will take the system back to the *Right Serve* state.

You will use the 16-bit bidirectional shift register from part one of the lab that was built with your 4-bit universal shift register components. This will be the game table.

Assume that the circular bi-directional shift register from part 1 has been modified as follows:

- All data inputs used in the *Load* mode are set to a logic level 0. No pattern is loaded from switches.
- The circular connection of the 16-bit universal shift register outputs are visible on the 16 center red LEDs and that the leftmost and rightmost LEDs display the ball to be served or the point scored. The 18 red LED display would show the following. P_x values are shift register outputs. *RE* holds the ball for a right serve and *LE* holds the ball that exits after moving left if not returned by a paddle.

<i>LE</i>	P_{15}	P_{14}	...	P_1	P_0	<i>RE</i>
-----------	----------	----------	-----	-------	-------	-----------

Design and simulate the controller for this limited activity of the one-dimensional Pong game. There are three inputs for this limited version. $reset$, $serve_r$ and P_{15} . The outputs will be RE , LE , and s_1 and s_0 which control the action of the bidirectional shift register.

Draw a state transition diagram for this 4-state system. For each state identify the values of the four outputs. For each state transition, identify the input values that will cause the transition.

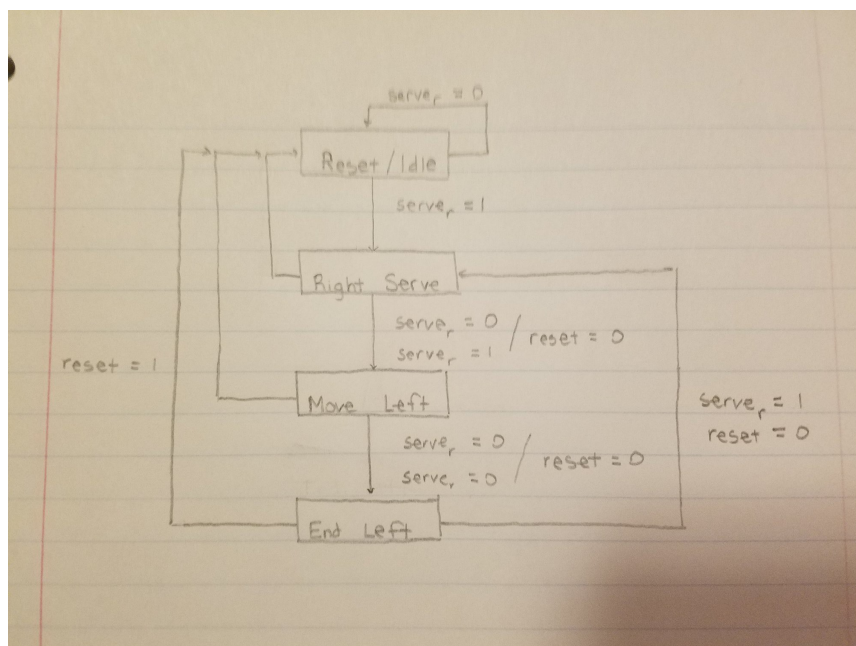


Figure 1: State Diagram for the One-Dimensional Pong game

From the last lab we had $s_1s_0 = 01$ as shift left and 10 as shift right. We will never be loading (11) . Holding is 00 .

At the *Idle* state, the output RE is 1 . And s_1s_0 is 00 .

At the *Right Serve* state, we are starting up to move left from the RE location. $RE = 1$ and $s_1s_0 = 01$.

At the *Move Left* state, we are moving left ($s_1s_0 = 01$) and the red LEDs will be lighting up in sequential order.

At the *End Left* state, we stopped moving ($s_1s_0 = 00$) and LE is now 1 .

Make a next state table using the symbolic names. Design a circuit to implement this system using four flip-flops—one for each state. Write the logic equations for the D inputs to each flip flop.

Present State	Next State
$Y_3 Y_2 Y_1 Y_0$	$D_3 D_2 D_1 D_0$

$$D_3 = \text{server}_r \cdot Y_3 \cdot Y_2 + \text{server}_r \cdot Y_2$$

$$D_2 = Y_1$$

$$D_1 = \text{serve}_r \cdot y_3 \cdot y_0$$

$$D_0 = \overline{\text{serve}}_r \cdot \gamma_0$$

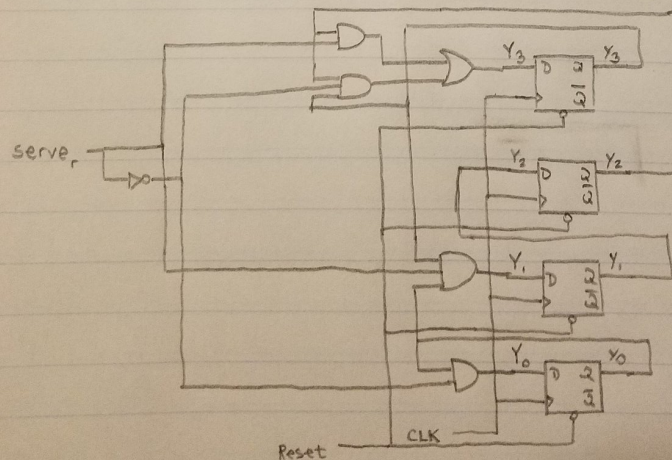


Figure 2: State Table, Logical Equations for D Inputs and Circuit Implementation

Show a hand drawn timing diagram for the operation of the controller for the case where a reset input is received and then a $serve_r$ input is received. For the purpose of the timing diagram, assume the shift register has a length of 4-i.e. only P_{15} P_{14} P_1 P_0 . On the timing diagram, show all the controller outputs P_{15} P_{14} P_1 P_0

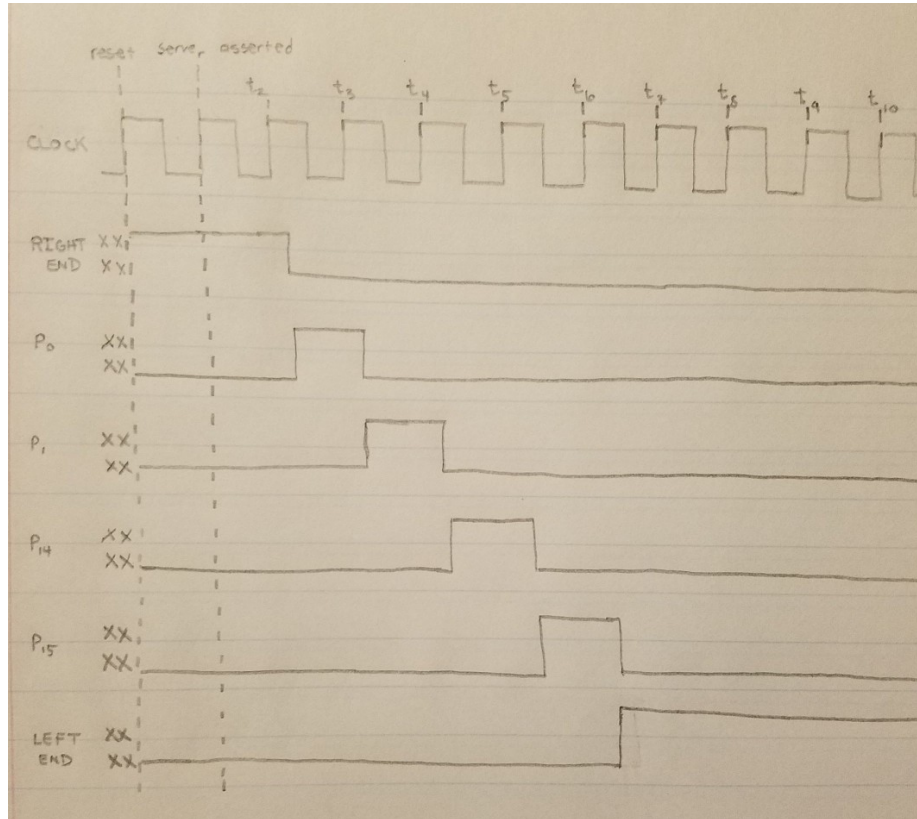


Figure 3: Timing Diagram of the Implemented Circuit